

202021025 안준영

정리형 과수님 논리회로 9-2 .

16x1 MUX - 27H

4x16 decoder → 17H

$$F = \sum_{m(0,1,5,6,9,14)}$$

