

	전압이득	전류이득	입력저항	출력저항
CS	$-g_m R_D$		$\infty$	$R_d$
CS with $R_s$	$\simeq -\frac{R_D}{R_S}$		$\infty$	$r_d$
CD	$\simeq 1$		$\infty$	$\simeq \frac{1}{g_m}$
CG	$\frac{g_m R_D}{1 + g_m R_{SS}}$	$\simeq 1$	$\frac{1}{g_m}$	$r_d$

1) 공통소스 증폭기

$$\text{전압이득 } A_v = \frac{v_o}{v_s} = \frac{-g_m v_{gs} R_D}{v_s} = -g_m R_D \quad (v_s = v_{gs})$$

$$\text{입력저항 } R_i = R_1 \parallel R_2 (>> R_S)$$

$$\text{출력저항 } R_o = R_D (r_d \text{ 무시하면})$$

2) 소스 저항을 갖는 공통소스 증폭기

$$\text{전압이득 } A_v = \frac{v_o}{v_s} = \frac{\frac{-g_m R_D}{1 + g_m R_S} v_g}{v_s} = \frac{-g_m R_D}{1 + g_m R_S} (v_s = v_g), \quad g_m R_S >> 1, \quad -\frac{R_D}{R_S}$$

3) 공통드레인 증폭기

$$\text{전압이득 } A_v = \frac{v_o}{v_s} = \frac{g_m \frac{v_s}{1 + g_m R_S} R_S}{v_s} = \frac{g_m R_S}{1 + g_m R_S} \simeq 1 (g_m R_S \gg 1)$$

$$\text{출력저항 } R_o \equiv \frac{v_t}{i_t} = \frac{-v_{gs}}{-g_m v_{gs}} = \frac{1}{g_m} \quad (R_o = r_d \parallel \frac{1}{g_m}, \quad r_d >> g_m) : \text{매우 작은 출력저항}$$

4) 공통드레인 증폭기

$$\text{전압이득 } A_v = \frac{v_o}{v_s} = \frac{-g_m (\frac{-v_s}{1 + g_m R_{SS}}) R_D}{v_s} = \frac{g_m R_D}{1 + g_m R_{SS}}$$

$$\text{전류이득 } A_i = \frac{i_o}{i_{ss}} = \frac{-g_m (\frac{-R_{SS}}{1 + g_m R_{SS}}) i_{ss}}{i_{ss}} = \frac{g_m R_{SS}}{1 + g_m R_{SS}} \simeq 1 (g_m R_{SS} \gg 1)$$

$$\text{입력저항 } R_i = \frac{-v_{gs}}{i_i} = \frac{-v_{gs}}{-g_m v_{gs}} = \frac{1}{g_m} : \text{매우 작은 입력저항}$$

$$\text{출력저항 } R_o = r_d, \rightarrow \infty : \text{매우 큰 출력저항} \Rightarrow \text{전류버퍼로 사용됨}$$