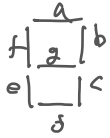


논리회로 과제 8-2



A: $d = 0$ ($\overline{1} \cdot \overline{1}$)

B: $a, b = 0$ ($\overline{1} \cdot \overline{1}$)

C: $a, b, c = 0$ ($\overline{1} \cdot \overline{1} \cdot \overline{1}$)

D: $a, f = 0$ ($\overline{1} \cdot \overline{1}$)

E: $b, c = 0$ ($\overline{1} \cdot \overline{1}$)

F: $b, c, d = 0$ ($\overline{1} \cdot \overline{1} \cdot \overline{1}$)

	A	B	C	D	a	b	c	d	e	f	g
A	1	0	1	0	1	1	1	0	1	1	1
B	1	0	1	1	0	0	1	1	1	1	1
C	1	1	0	0	1	0	0	1	1	1	0
D	1	1	0	1	0	1	1	1	1	0	1
E	1	1	1	0	1	0	0	1	1	1	1
F	1	1	1	1	1	0	0	0	1	1	1