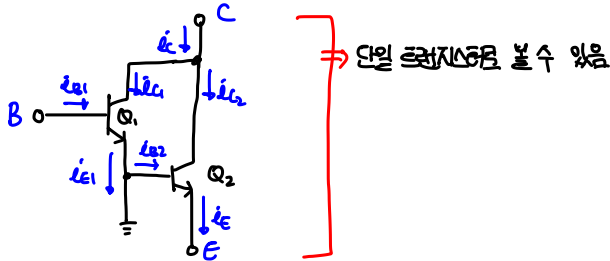


CC-CC 종속 연립 근. 단일트 쌍, 복합 트랜지스터



$$\bullet i_{E1} = (\beta_{02} + 1) i_{B1} = i_{B2}$$

$$\bullet i_{C2} = \beta_{02} \cdot i_{B2} = \beta_{02} \cdot (\beta_{01} + 1) i_{B1}$$

$$\begin{aligned} \bullet i_C &= i_{C1} + i_{C2} \\ &= [\beta_{01} \cdot i_{B1}] + [\beta_{02} \cdot (\beta_{01} + 1) \cdot i_{B1}] \\ &= [\beta_{01} + \beta_{02} \cdot (\beta_{01} + 1)] \cdot i_{B1} \end{aligned}$$

$$\therefore \beta_{DP} = \frac{i_C}{i_{B1}} = \beta_{01} + \beta_{02} (\beta_{01} + 1) \cong \beta_{01} \cdot \beta_{02} \quad \Rightarrow \text{두 트랜지스터의 곱으로, 매우 큰 전류 이득을 얻을 수 있다.}$$

$$\therefore \text{if } \beta_{01} = \beta_{02} = \beta_0, \beta_{DP} = \beta_0^2$$