

2022/02/19 25 안준영

정기현 교수님 논리회로 9-1

8x1MUX 2개 → 16x1MUX

